

ECE 5722 Homework 1

By Bruce Huynh


9/5/2021

Introduction:

In this assignment we were tasked to build a sequence detector that would detect the sequence: “10110” and output high on w if it detected it. Afterwards, a counter would be initiated that counts 32 clock cycles and flows back into the sequence detector to tell it to start finding the sequence once again.


A.) State Diagram:

 To easily find inputs and outputs necessary for the sequence detector, a state diagram is needed. At each state, it can receive a 1 or 0 which leads it to the next state. Knowing this, I mapped out each state.



B.)

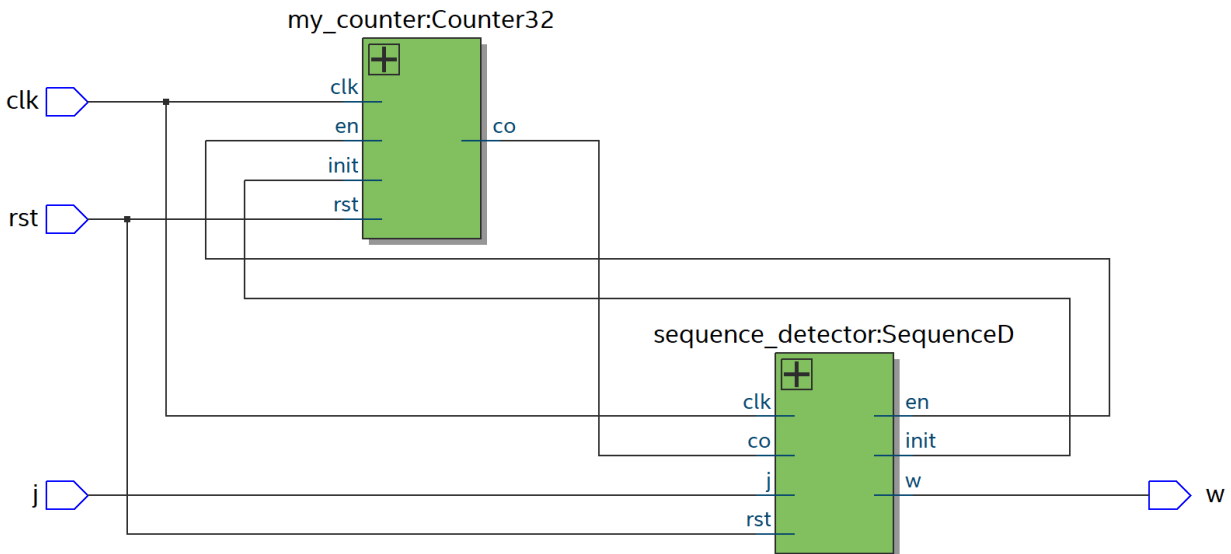The following is the top-level RTL design:



The accompanying code for the top-level module:

```

module moore_with_counter(input j, clk, rst, output w);

    wire detector_en_to_counter;
    wire detector_init_to_counter;
    wire counter_clockout_to_detector;

    my_counter Counter32 (.clk (clk), .rst (rst), .en
(detector_en_to_counter), .init (detector_init_to_counter), .co
(counter_clockout_to_detector));

    sequence_detector SequenceD (.j (j), .clk (clk), .rst (rst),
.co (counter_clockout_to_detector), .w (w), .init
(detector_init_to_counter), .en (detector_en_to_counter));

endmodule

```

Code for the sequence detector:

```
module sequence_detector(input j, clk, rst, co, output w, init, en);

    parameter [4:0] reset = 3'b000, got1 = 3'b001, got10 = 3'b010,
    got101 = 3'b011, got1011 = 3'b100, got10110 = 3'b101;
    reg[4:0] pres_state, next_state;
    reg[7:0] firsttime; //variable to detect first j input
    reg pulse, outputon;
    //pulse enables the module to run
    //outputon is the output of the system that is kept high until
    //the module is initiated again

    initial firsttime = 0;

    always @ (posedge clk) begin
        firsttime = firsttime + 1;
        //detects either the clock out from the counter or the
        //first time j is detected
        if (co == 1 || firsttime == 1) begin
            pulse = 1;
            outputon = 0;
        end
        if (next_state == got10110) begin
            pulse = 0;
            outputon = 1;
        end
        //no longer the first time after this if statement
        if (firsttime == 8'b11111111)

            firsttime = 8'b00000010;

    end
    //state machine logic
    always @ (pres_state or j) begin : combinational
        next_state = 0;
    end
endmodule
```

```
if (pulse == 1) begin
    case (pres_state)

        reset: begin
            if (j == 1'b1)
                next_state = got1;
            else
                next_state = reset;
            end

        got1: begin
            if (j == 1'b0)
                next_state = got10;
            else
                next_state = got1;
            end

        got10: begin
            if (j == 1)
                next_state = got101;
            else
                next_state = reset;
            end

        got101: begin
            if (j == 1)
                next_state = got1011;
            else
                next_state = got10;
            end

        got1011: begin
            if (j == 0)
                next_state = got10110;
            else
                next_state = got1;
            end

        got10110: begin
```

```

        if (j == 0)
            next_state = reset;
        else
            next_state = got101;
        end

        default next_state = reset;

    endcase
end

end

always @ (posedge clk or posedge rst) begin
    if (rst)
        pres_state <= reset;
    else
        pres_state <= next_state;
    end

    assign w = outputon;
    assign init = (pres_state == got10110) ? 1 : 0; //tells the
counter when to start

    assign en = w; //enables the counter

endmodule

```

Code for the counter:

```

module my_counter (input clk, rst, en, init, output co);

reg [5:0] current;
reg pulse;

```

```

always @ (posedge clk) begin

    if (init)
        pulse = 1'b1; //keeps counter

    if (current == 6'b100000)
        pulse = 1'b0; //counter is off after 32 clock cycles
end

always @ (posedge clk) begin

    if (rst || current == 6'b100000)
        current <= 6'b000000;
    else if (en && pulse)
        current = current + 1'b1; //counting mechanism
end

assign co = (current == 6'b100000) ? 1 : 0; //counter output

endmodule

```

C.) Testbenches

For each of the smaller modules, I made testbenches for them. Very similar testbenches will be used in the top-level module.

Sequence detector (fixed “10110”) test:

```

module sequence_detector_test_fixed;

    reg j, clk, rst, co;
    wire w, init, en;

    sequence_detector uut (j, clk, rst, co, w, init, en);

```

```

initial begin

    co = 1'b1; clk = 1'b1; rst = 1'b1; j = 1'b1;

end


initial #5 rst = 1'b0;
initial #5 co = 1'b0;
always #30 clk = ~clk;

always begin
    j = 1'b1; #60; j = 1'b0; #60; j = 1'b1; #60; j = 1'b1; #60; j =
    1'b0; #60; #1200; co = 1'b1; #2; co = 1'b0;
end


```

Waveform:

(order: j, clk, co, w, init, en, rst)

 

 The module is initialized with a small pulse from *co* (clock out from the counter). When the module detects “10110”, *init* is pulsed while *w* and *en* is driven high.



When *co* is pulsed again, the cycle continues like seen above.

Sequence detector with random j inputs test:

```

module sequence_detector_test_rdm;

    reg j, clk, rst, co;
    wire w, init, en;

    sequence_detector uut (j, clk, rst, co, w, init, en);

    initial begin

        co = 1'b1; clk = 1'b1; rst = 1'b1; j = 1'b0;

    end

    initial #25 rst = 1'b0;
    initial #10 co = 1'b0;


    always #30 clk = ~clk;
    always #15 j = $random;

endmodule

```

Waveform:

(order: j, clk, co, w, init, en, rst)

 

The module is receiving random inputs and waits until it gets “10110” in which it pulses *init* and turns *w* and *en* high.

Counter test:

```

module my_counter_test;
    reg clk, rst, en, init;
    reg current, pulse;
    wire co;
    my_counter uut (clk, rst, en, init, co);

    initial begin
        clk = 1'b0;
        rst <= 1'b1;
        #5 rst <= 1'b0;
        #10 en <= 1'b1;
        init = 1'b1;
    end

    always @ (posedge clk) begin
        #20 init = 1'b0;
        #2000;
        #20 init = 1'b1;
        #20 init = 1'b0;
    end


    always #5 clk = ~clk;

endmodule

```

Waveform:

 (order: clk, rst, en, init, co, current, pulse)



When we have a constant *en* and an *init* pulse, the clock will begin to count. It will count up to 32 (8'b10000000) where it will pulse *co* and then stop counting until it is initiated again.

Top-level testbench (moore_with_counter):

Like mentioned earlier, the top-level module uses the same test as the sequence detector as seen below:

Fixed pattern:

```
module moore_with_counter_test_fixed;

    reg j, clk, rst;
    wire w;

    moore_with_counter uut (j, clk, rst, w);

    initial begin

        clk = 1'b1; rst = 1'b1; j = 1'b1;

    end

    initial #5 rst = 1'b0;
    always #30 clk = ~clk;
```

```


        always begin
            j = 1'b1; #60; j = 1'b0; #60; j = 1'b1; #60; j = 1'b1; #60; j =
1'b0; #60;
        end

endmodule

```

Waveform:

(order: j, clk, rst, w)

 

As seen in the waveform, when the first j input is received, the module will start looking for the “10110” sequence. Once it has found it, w gets turned on and stays on for 32 clock cycles. After that, w turns off and the search begins once again. The pattern above is fixed and shows w being high twice. If you count the clock pulses after w gets turned on high, you will be able to count 32 clock pulses.

Random pattern:

```

module moore_with_counter_test_rdm;

    reg j, clk, rst, co;
    wire w;

    moore_with_counter uut (j, clk, rst, w);

    initial begin

        clk = 1'b1; rst = 1'b1; j = 1'b0;

```

```

end

initial #25 rst = 1'b0;


always #30 clk = ~clk;
always #15 j = $random;

endmodule

```

Waveform:

(order: j, clk, rst, w)

 

Like earlier, the module will detect “10110” and output high on w when it does. w remains high until 32 counts where it will go back to 0. The search will continue until the sequence is detected again. The waveform above shows this happening twice with random j inputs. If you count the clock pulses after w gets turned on high, you will be able to count 32 clock pulses.

Synthesis:

Analysis & Synthesis Summary

 <<Filter>>

Analysis & Synthesis Status	Successful - Sun Sep 05 17:57:42 2021
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	hw1
Top-level Entity Name	moore_with_counter
Family	Cyclone V
Logic utilization (in ALMs)	N/A
Total registers	22
Total pins	4
Total virtual pins	0
Total block memory bits	0
Total DSP Blocks	0
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0
Total DLLs	0